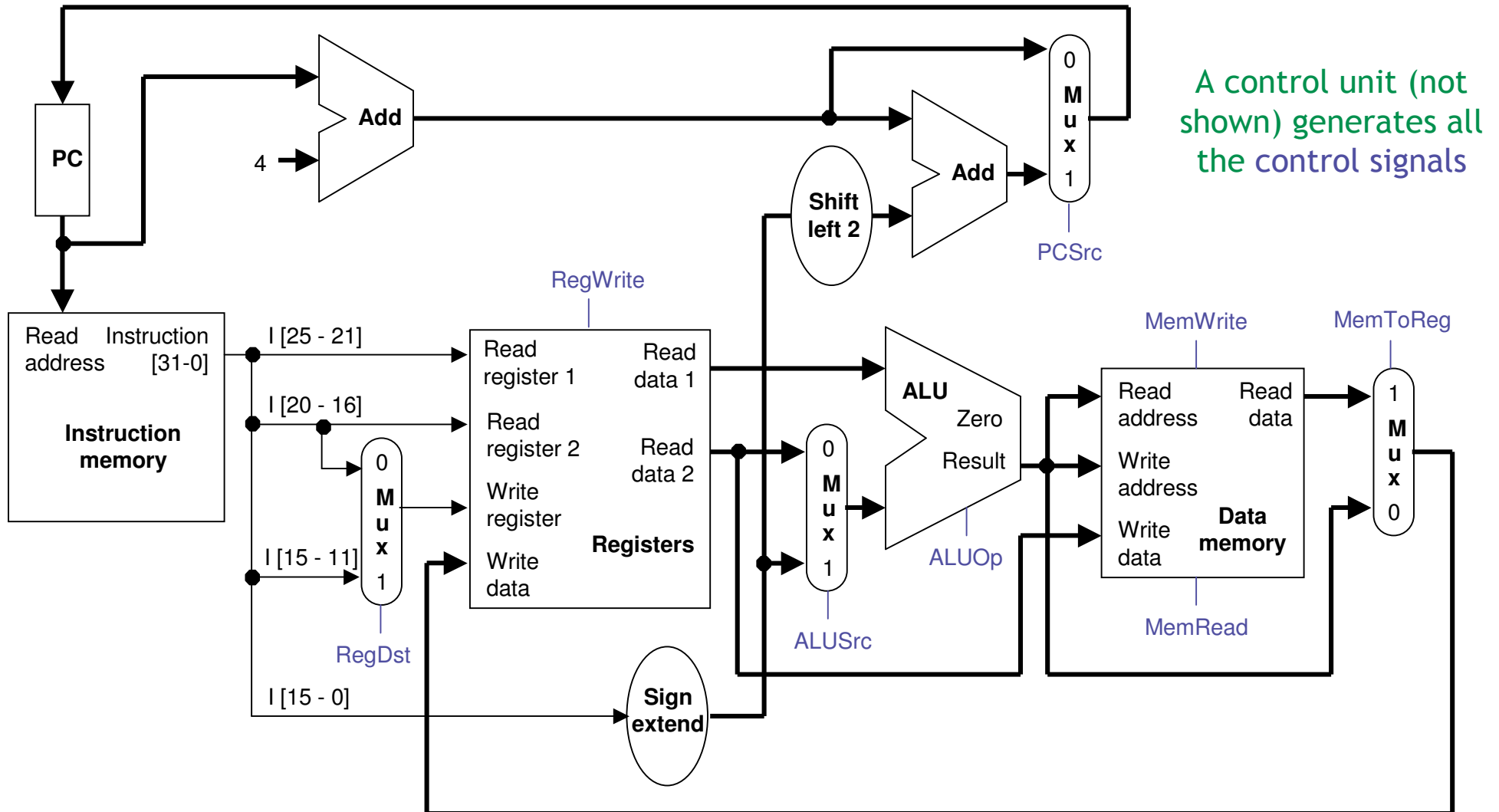



# The single-cycle design from last time



\_\_\_\_\_



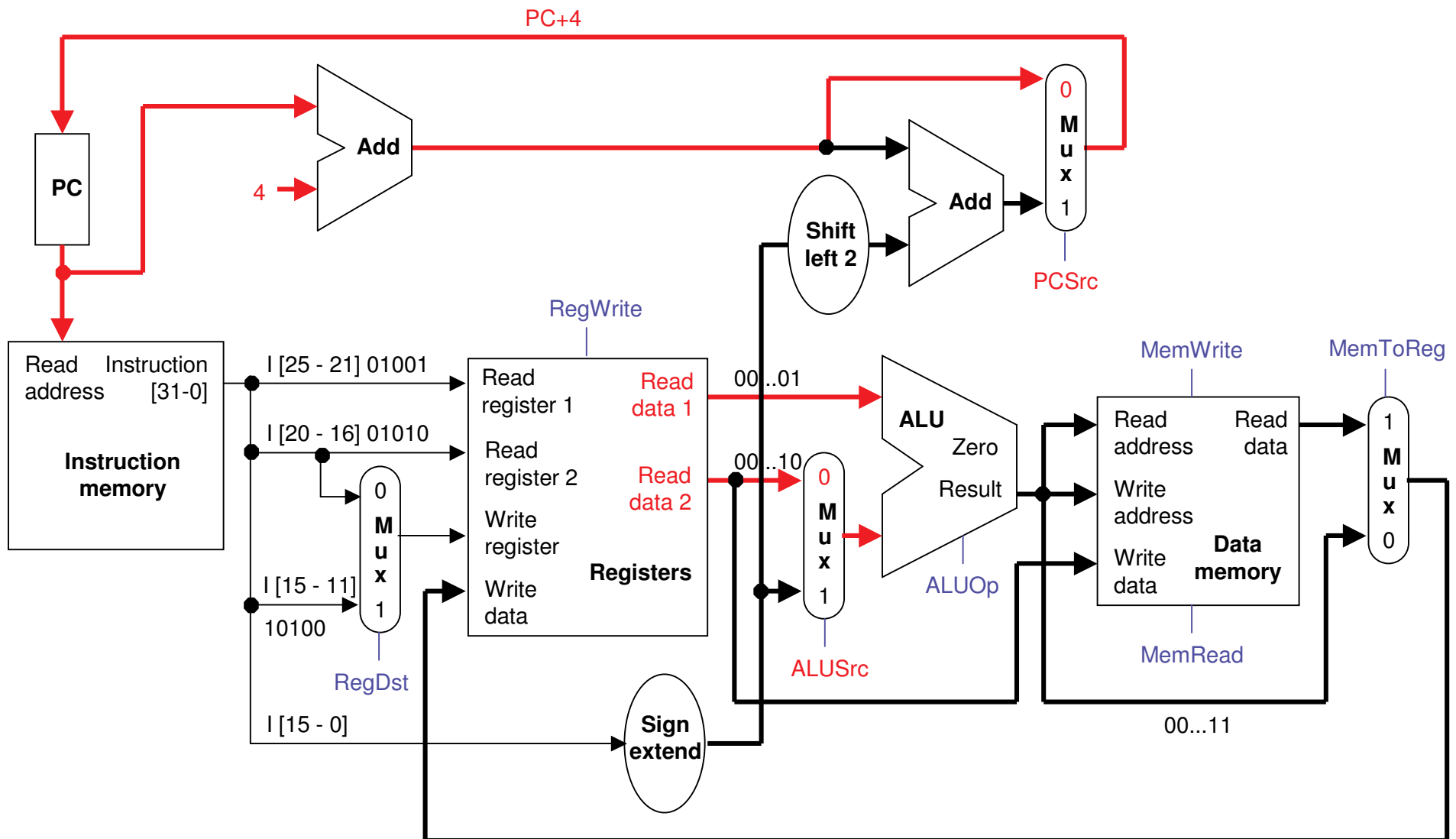
# How `add $s4, $t1, $t2` goes through the datapath



Read registers, increment PC + 4, set new PC
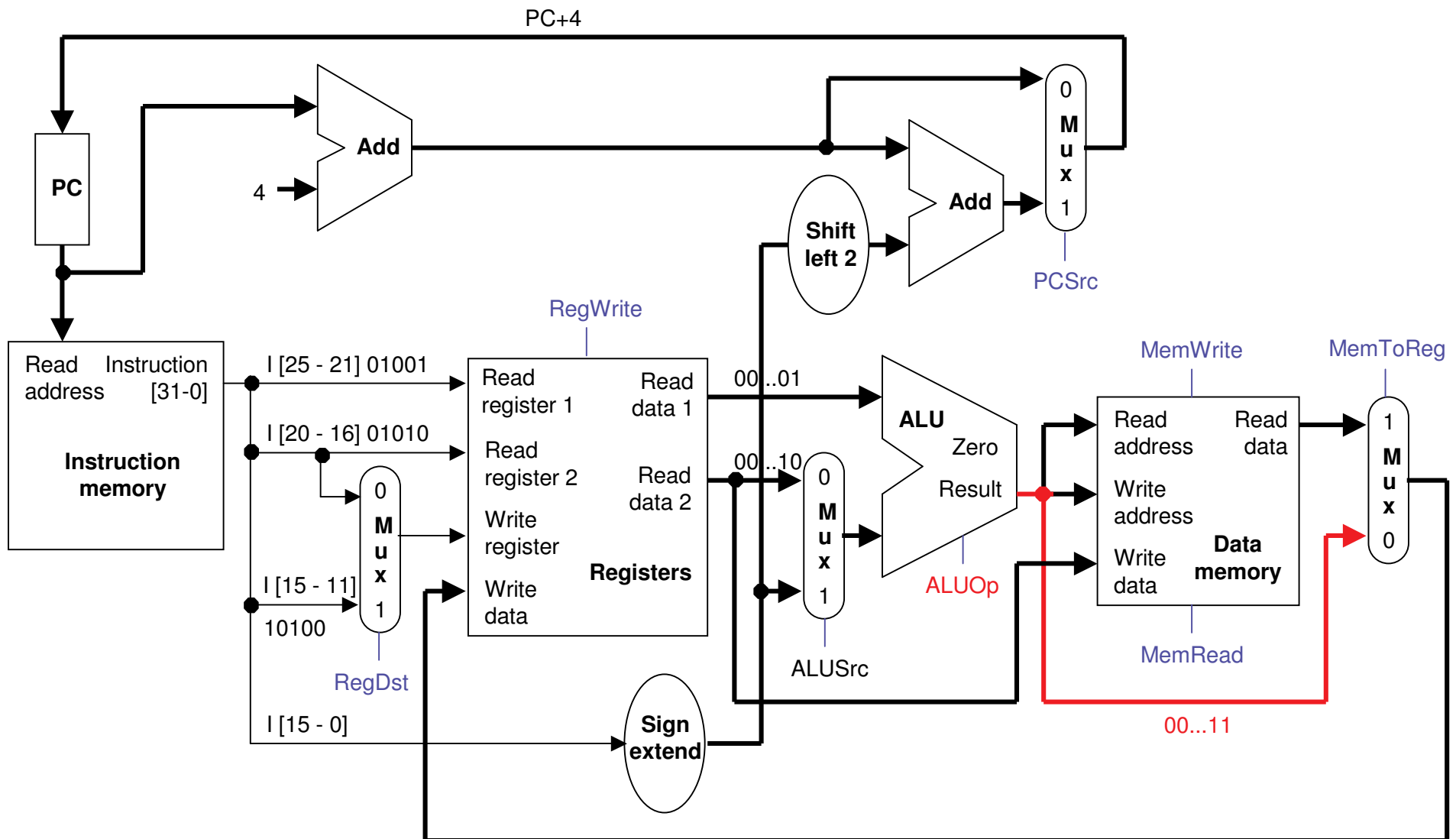
# How `add $s4, $t1, $t2` goes through the datapath







Perform addition in ALU

\_\_\_\_\_
    
# Timing issues: clock edges

- In an instruction like `add $t1, $t1, $t2`, how do we know \$t1 is not updated until *after* its original value is read?
- We'll assume that our state elements are **positive edge triggered**, and are updated only on the positive edge of a clock signal.
  - The register file and data memory have explicit write control signals, **RegWrite** and **MemWrite**. These units can be written to only if the control signal is asserted *and* there is a positive clock edge.
  - In a single-cycle machine the PC is updated on each clock cycle, so we don't bother to give it an explicit write control signal.



# Performance of Single-cycle Design

---

$$\text{CPU time}_{x,p} = \text{Instructions executed}_p * \text{CPI}_{x,p} * \text{Clock cycle time}_x$$

CPI = 1 for a single-cycle design


1. On a positive clock edge, the PC is updated with a new address.
  2. A new instruction can then be loaded from memory. The control unit sets the datapath signals appropriately so that
    - registers are read,
    - ALU output is generated,
    - data memory is read for a lw instruction, and
    - branch target addresses are computed.
  3. Several things happen on the *next* positive clock edge.
    - The register file is updated for arithmetic or lw instructions.
    - Data memory is written for a sw instruction.
    - The PC is updated to point to the next instruction.
- In a **single-cycle datapath** everything in Step 2 must complete within one clock cycle, before the next positive clock edge.

*How long is that clock cycle?*

# Components of the data-path

- If all instructions must complete within one clock cycle, then the cycle time has to be large enough to accommodate the *slowest* instruction.
- Each component of the datapath has an associated *delay* (latency)

reading the instruction memory	2ns	}	8ns
reading the register file	1ns		
ALU computation	2ns		
accessing data memory	2ns		
writing to the register file	1ns		

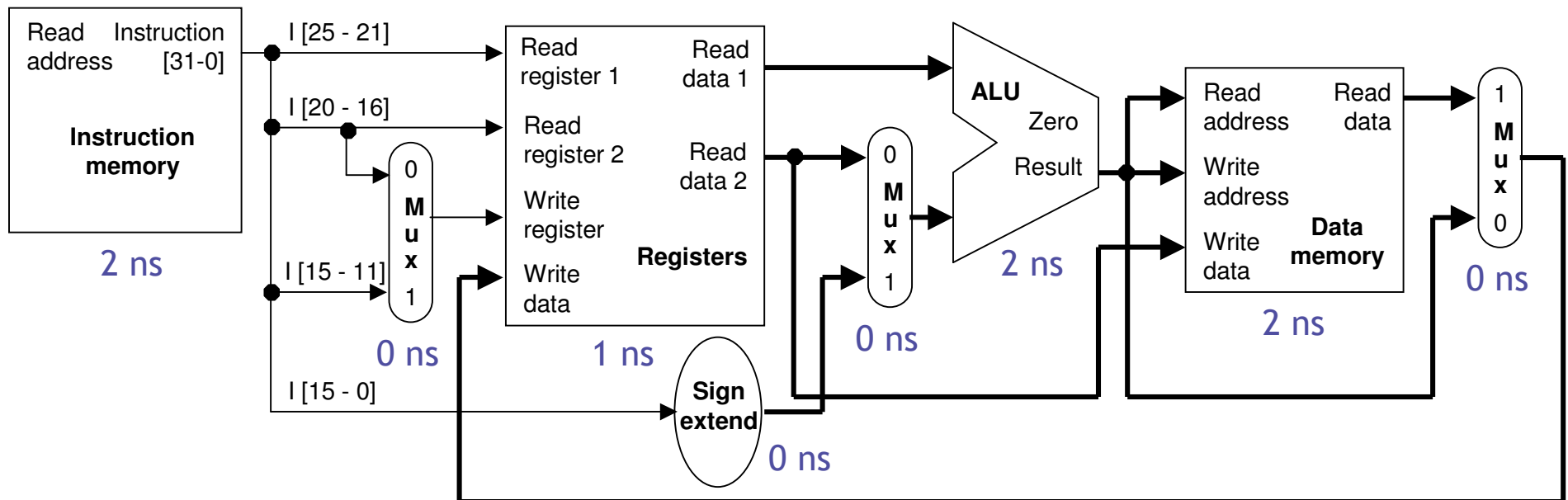




# The slowest instruction...

- A lw instruction uses *all* components of the datapath
- For example, `lw $t0, -4($sp)` needs 8ns, assuming the delays shown here.

reading the instruction memory	2ns	} 8ns
reading the base register \$sp	1ns	
computing memory address \$sp-4	2ns	
reading the data memory	2ns	
storing data back to \$t0	1ns	

 


## ...determines the clock cycle time

- If we make the cycle time 8ns then *every* instruction will take 8ns, even if they don't need that much time.
- For example, the instruction `add $s4, $t1, $t2` really needs just 6ns.

reading the instruction memory      2ns  
reading registers \$t1 and \$t2      1ns  
computing \$t1 + \$t2      2ns  
storing the result into \$s0      1ns


} 6ns

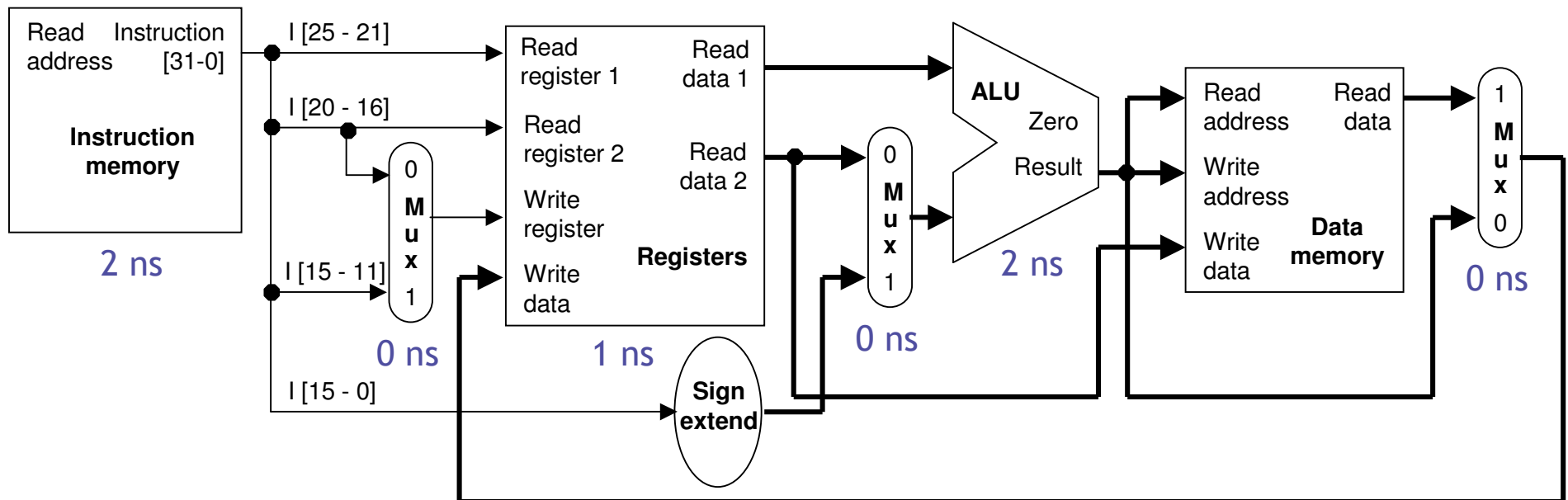

# How bad is this?

- With these same component delays, a **sw** instruction would need 7ns, and **beq** would need just 5ns.
- Let's consider the **gcc** instruction mix from p. 189 of the textbook.

Instruction	Frequency
Arithmetic	48%
Loads	22%
Stores	11%
Branches	19%

 

- With a single-cycle datapath, each instruction would require 8ns.
- But if we could execute instructions as fast as possible, the average time per instruction for gcc would be:

$$(48\% \times 6\text{ns}) + (22\% \times 8\text{ns}) + (11\% \times 7\text{ns}) + (19\% \times 5\text{ns}) = 6.36\text{ns}$$

- The single-cycle datapath is about 1.26 times slower!

## It gets worse...

---

- We've made very optimistic assumptions about memory latency:
  - Main memory accesses on modern machines is  $>50\text{ns}$ .
  - For comparison, an ALU operation on the Pentium4 takes  $\sim 0.3\text{ns}$ .
- Our worst case cycle (loads/stores) includes 2 memory accesses
  - A modern single cycle implementation would be stuck at  $<10\text{Mhz}$ .
  - Caches will improve common case access time, not worst case.
- Tying frequency to worst case path violates first law of performance!!

# Improving performance

---


- Two ideas for improving performance:
  1. Split each instruction into multiple steps, each taking 1 cycle
    - steps: IF (instruction fetch), ID (instruction decode), EX (execute ALU operation), MEM (memory access), WB (register write-back)
    - slow instructions take more cycles than fast instructions
    - known as a *multi-cycle* implementation
  2. Crucial observation: each instruction uses only a *portion* of the datapath in each step
    - can *overlap* instructions; each uses one portion of the datapath
    - known as a *pipelined* implementation
- Examples of pipelining: any assembly process (cars, sandwiches), multiple loads of laundry (washer + dryer can be pipelined), etc.
 
# Pipelining: a SPIMbot example

- The basic operation can be broken into three steps:
  - Do Scan (DS), which initiates a scan
  - Scan Handler (SH), which processes the scan
  - Get Tokens (GT), which picks the tokens up
- Our current implementation is “multi-cycle”




- Key observation:
  - SH must finish before next SH starts (since both write to the same memory address)...
  - ... but DS can start as soon as previous SH is complete
- Thus, we can overlap DS and GT:




# Implementing simple pipeline

- Multi-cycle implementation:

 


- Pipelined implementation:

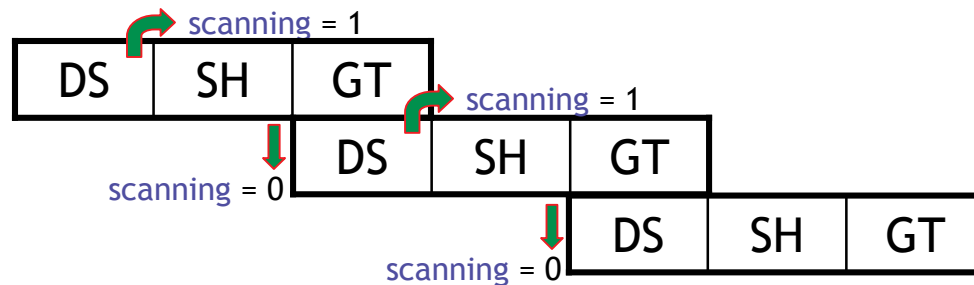
 
## A complication: GT can be slow

- In SH, we determine `scan_length` and set `index` to zero
- So, the following situation is bad since SH interferes with GT



- How can we avoid this problem?

Change the code in SH so that each new token found is placed at the *back of a queue*. The easiest way to implement queues is as arrays. Treat `xcoord` and `ycoord` as queues by adding new tokens to the end (and increase `scan_length` by 1). In GT, once `index` equals `scan_length` (i.e. all tokens in the queue are found), simply set `index` and `scan_length` to 0.

- We can now potentially pipeline even better...

